


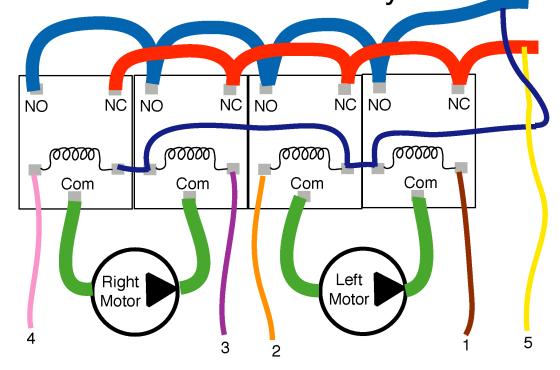
If the coil voltage and the motor voltage is the same then use this layout



SPDT 5v 15amp Relay

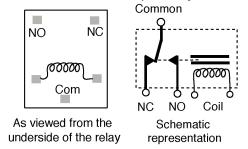

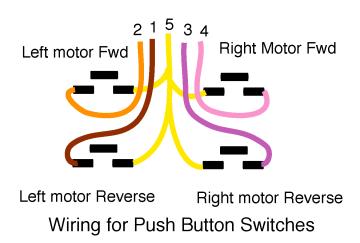

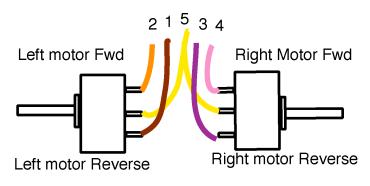

Wiring for SPDT Momentary Toggle Switches